

Міністерство освіти і науки України
Національний університет «Львівська політехніка»

Кафедра ЕОМ



Звіт

до лабораторної роботи № 3

з дисципліни «Моделювання комп'ютерних систем»
на тему:

«Поведінковий опис цифрового автомата Перевірка роботи автомата за
допомогою стенда Elbert V2 – Spartan 3A FPGA»

Варіант №22

Виконав:
ст. гр. КІ-201
Погребняк А. Ю.
Прийняв:
ст. викладач
каф. ЕОМ
Козак Н. Б.

Львів 2024

Мета роботи: На базі стенда реалізувати цифровий автомат для обчислення значення виразів.

Виконання роботи:

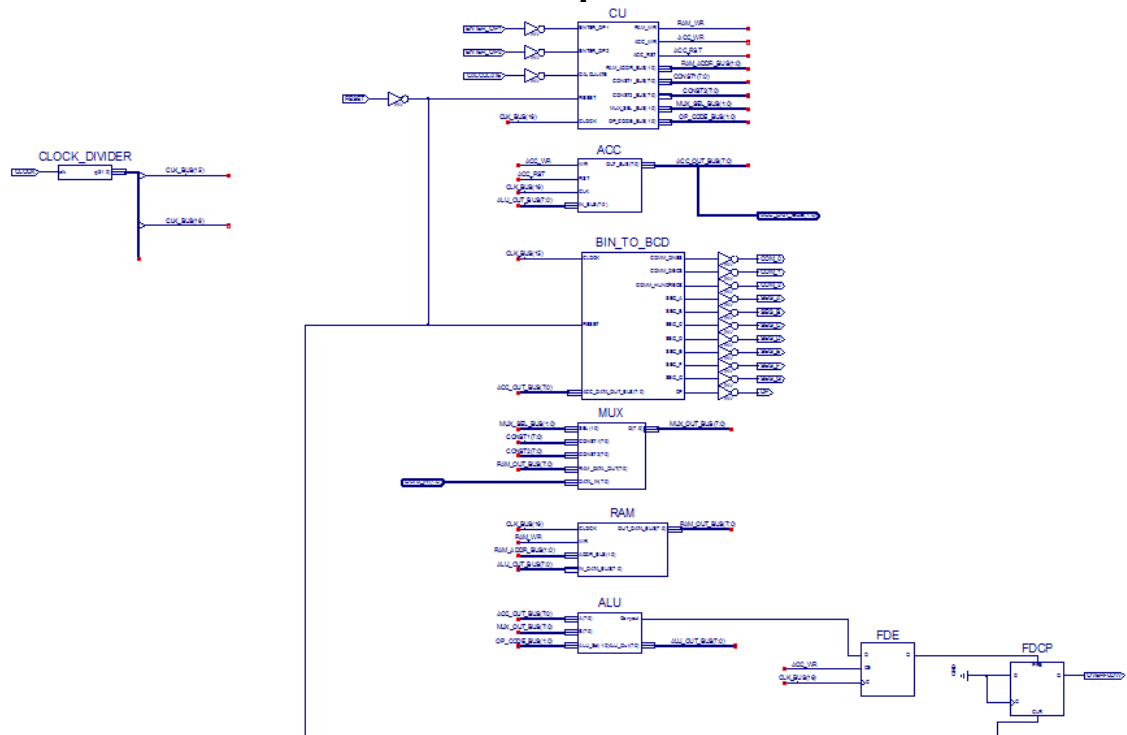


Рис. 1 – Top Level

Файл ACC.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity ACC is
```

```
    Port ( WR : in STD_LOGIC;
```

```
          RST : in STD_LOGIC;
```

```
          CLK : in STD_LOGIC;
```

```
          IN_BUS : in STD_LOGIC_VECTOR (7 downto 0);
```

```
          OUT_BUS : out STD_LOGIC_VECTOR (7 downto 0));
```

```
end ACC;
```

```
architecture ACC_arch of ACC is
```

```
    signal DATA : STD_LOGIC_VECTOR (7 downto 0);
```

```
begin
```

```
    process (CLK)
```

```
    begin
```

```

    if rising_edge(CLK) then
        if RST = '1' then
            DATA <= (others => '0');
        elsif WR = '1' then
            DATA <= IN_BUS;
        end if;
    end if;
end process;

```

```

    OUT_BUS <= DATA;

```

```

end ACC_arch;

```

Файл ALU.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use ieee.NUMERIC_STD.all;
entity ALU is
    Port (
        A, B      : in  STD_LOGIC_VECTOR(7 downto 0);
        ALU_Sel   : in  STD_LOGIC_VECTOR(1 downto 0);
        ALU_Out   : out STD_LOGIC_VECTOR(7 downto 0);
        Carryout  : out std_logic
    );
end ALU;
architecture Behavioral of ALU is

    signal ALU_Result : std_logic_vector (15 downto 0);

begin
    process(A,B,ALU_Sel)
    begin
        case(ALU_Sel) is
            when "01" =>
                ALU_Result <= ("00000000" & A) + ("00000000" & B);
            when "10" =>
                ALU_Result <=
                    std_logic_vector(to_unsigned((to_integer(unsigned(("00000000" & A))) *
                    to_integer(unsigned(("00000000" & B)))),16)) ;
            when "11" =>
                case(B) is

```

```

        when x"00" => ALU_Result <=
std_logic_vector(unsigned(("00000000" & A)) sll 0);
        when x"01" => ALU_Result <=
std_logic_vector(unsigned(("00000000" & A)) sll 1);
        when x"02" => ALU_Result <=
std_logic_vector(unsigned(("00000000" & A)) sll 2);
        when x"03" => ALU_Result <=
std_logic_vector(unsigned(("00000000" & A)) sll 3);
        when x"04" => ALU_Result <=
std_logic_vector(unsigned(("00000000" & A)) sll 4);
        when x"05" => ALU_Result <=
std_logic_vector(unsigned(("00000000" & A)) sll 5);
        when x"06" => ALU_Result <=
std_logic_vector(unsigned(("00000000" & A)) sll 6);
        when x"07" => ALU_Result <=
std_logic_vector(unsigned(("00000000" & A)) sll 7);
        when others => ALU_Result <=
std_logic_vector(unsigned(("00000000" & A)) sll 0);
    end case;
    ALU_Result(15 downto 8) <= "00000000";
    when others => ALU_Result <= ("00000000" & B);
    end case;
end process;
ALU_Out <= ALU_Result(7 downto 0);
Carryout <= ALU_Result(8) OR ALU_Result(9) OR ALU_Result(10) OR
ALU_Result(11) OR ALU_Result(12) OR ALU_Result(13) OR
ALU_Result(14) OR ALU_Result(15);
end Behavioral;

```

Файл CPU.vhd

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity CU is

port(ENTER_OP1 : IN STD_LOGIC;

ENTER_OP2 : IN STD_LOGIC;

CALCULATE : IN STD_LOGIC;

RESET : IN STD_LOGIC;

CLOCK : IN STD_LOGIC;

RAM_WR : OUT STD_LOGIC;

RAM_ADDR_BUS : OUT STD_LOGIC_VECTOR(1 DOWNT0 0);

CONST1_BUS : OUT STD_LOGIC_VECTOR(7 DOWNT0 0);

```

CONST2_BUS : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
ACC_WR : OUT STD_LOGIC;
ACC_RST : OUT STD_LOGIC;
MUX_SEL_BUS : OUT STD_LOGIC_VECTOR(1 DOWNTO 0);
OP_CODE_BUS : OUT STD_LOGIC_VECTOR(1 DOWNTO 0));
end CU;

architecture CU_arch of CU is

type STATE_TYPE is (RST, IDLE, LOAD_OP1, LOAD_OP2,
RUN_CALC0, RUN_CALC1, RUN_CALC2, RUN_CALC3, RUN_CALC4,
FINISH);
signal CUR_STATE : STATE_TYPE;
signal NEXT_STATE : STATE_TYPE;

begin
CONST1_BUS <= "00000001";
CONST2_BUS <= "00001010";

SYNC_PROC: process (CLOCK)
begin
if (rising_edge(CLOCK)) then
if (RESET = '1') then
CUR_STATE <= RST;
else
CUR_STATE <= NEXT_STATE;
end if;
end if;
end process;

NEXT_STATE_DECODE: process (CUR_STATE, ENTER_OP1,
ENTER_OP2, CALCULATE)
begin
--declare default state for next_state to avoid latches
NEXT_STATE <= CUR_STATE; --default is to stay in current state
--insert statements to decode next_state
--below is a simple example
case(CUR_STATE) is
when RST =>
NEXT_STATE <= IDLE;
when IDLE =>

```

```

    if (ENTER_OP1 = '1') then
        NEXT_STATE <= LOAD_OP1;
    elsif (ENTER_OP2 = '1') then
        NEXT_STATE <= LOAD_OP2;
    elsif (CALCULATE = '1') then
        NEXT_STATE <= RUN_CALC0;
    else
        NEXT_STATE <= IDLE;
    end if;
when LOAD_OP1 =>
    NEXT_STATE <= IDLE;
when LOAD_OP2 =>
    NEXT_STATE <= IDLE;
when RUN_CALC0 =>
    NEXT_STATE <= RUN_CALC1;
when RUN_CALC1 =>
    NEXT_STATE <= RUN_CALC2;
when RUN_CALC2 =>
    NEXT_STATE <= RUN_CALC3;
when RUN_CALC3 =>
    NEXT_STATE <= RUN_CALC4;
when RUN_CALC4 =>
    NEXT_STATE <= FINISH;
when FINISH =>
    NEXT_STATE <= FINISH;
when others =>
    NEXT_STATE <= IDLE;
end case;
end process;
OUTPUT_DECODE: process (CUR_STATE)
begin
    case(CUR_STATE) is
        when RST =>
            MUX_SEL_BUS <= "00";
            OP_CODE_BUS <= "00";
            RAM_ADDR_BUS <= "00";
            RAM_WR <= '0';
            ACC_RST <= '1';
            ACC_WR <= '0';
        when IDLE =>
            MUX_SEL_BUS <= "00";
            OP_CODE_BUS <= "00";
            RAM_ADDR_BUS <= "00";

```

```

RAM_WR    <= '0';
ACC_RST   <= '0';
ACC_WR    <= '0';
when LOAD_OP1 =>
    MUX_SEL_BUS <= "00";
    OP_CODE_BUS <= "00";
    RAM_ADDR_BUS <= "00";
    RAM_WR      <= '1';
    ACC_RST     <= '0';
    ACC_WR      <= '1';
when LOAD_OP2 =>
    MUX_SEL_BUS <= "00";
    OP_CODE_BUS <= "00";
    RAM_ADDR_BUS <= "01";
    RAM_WR      <= '1';
    ACC_RST     <= '0';
    ACC_WR      <= '1';
when RUN_CALC0 =>
    MUX_SEL_BUS <= "01";
    OP_CODE_BUS <= "00";
    RAM_ADDR_BUS <= "01";
    RAM_WR      <= '0';
    ACC_RST     <= '0';
    ACC_WR      <= '1';
when RUN_CALC1 =>
    MUX_SEL_BUS <= "01";
    OP_CODE_BUS <= "10";
    RAM_ADDR_BUS <= "00";
    RAM_WR      <= '0';
    ACC_RST     <= '0';
    ACC_WR      <= '1';
when RUN_CALC2 =>
    MUX_SEL_BUS <= "10";
    OP_CODE_BUS <= "11";
    RAM_ADDR_BUS <= "00";
    RAM_WR      <= '0';
    ACC_RST     <= '0';
    ACC_WR      <= '1';
when RUN_CALC3 =>
    MUX_SEL_BUS <= "01";
    OP_CODE_BUS <= "01";
    RAM_ADDR_BUS <= "00";
    RAM_WR      <= '0';

```

```

    ACC_RST    <= '0';
    ACC_WR     <= '1';
when RUN_CALC4 =>
    MUX_SEL_BUS <= "11";
    OP_CODE_BUS <= "01";
    RAM_ADDR_BUS <= "00";
    RAM_WR     <= '0';
    ACC_RST    <= '0';
    ACC_WR     <= '1';
when FINISH  =>
    MUX_SEL_BUS <= "00";
    OP_CODE_BUS <= "00";
    RAM_ADDR_BUS <= "00";
    RAM_WR     <= '0';
    ACC_RST    <= '0';
    ACC_WR     <= '0';
when others  =>
    MUX_SEL_BUS <= "00";
    OP_CODE_BUS <= "00";
    RAM_ADDR_BUS <= "00";
    RAM_WR     <= '0';
    ACC_RST    <= '0';
    ACC_WR     <= '0';
end case;
end process;
end CU_arch;

```

```

Файл MUX.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MUX_Testbench is
end MUX_Testbench;

architecture Behavioral of MUX_Testbench is
    -- Constants

    -- Signals
    signal SEL : std_logic_vector(1 downto 0) := "00";
    signal CONST1 : std_logic_vector(7 downto 0) := (others => '0');
    signal CONST2 : std_logic_vector(7 downto 0) := (others => '1');

```



```

signal RAM_DATA_OUT : std_logic_vector(7 downto 0) := (others =>
'0');
signal DATA_IN : std_logic_vector(7 downto 0) := (others => '1');
signal O : std_logic_vector(7 downto 0);

begin

-- Stimulus process
stimulus: process
begin
-- Test case 1
SEL <= "00";
CONST1 <= "00001100";
CONST2 <= "01010101";
RAM_DATA_OUT <= "11110000";
DATA_IN <= "11111111";
wait for 10 ms;
-- Test case 2
SEL <= "01";
wait for 10 ms;

-- Test case 3
SEL <= "10";
wait for 10 ms;

-- Test case 4
SEL <= "11";
wait for 10 ms;

-- Add more test cases as needed

wait;
end process;

-- Instantiate the MUX
UUT: entity work.MUX
port map(
    SEL => SEL,
    CONST1 => CONST1,
    CONST2 => CONST2,
    RAM_DATA_OUT => RAM_DATA_OUT,
    DATA_IN => DATA_IN,
    O => O

```

```
);
```

```
end Behavioral;
```

Файл RAM.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.NUMERIC_STD.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity RAM is
```

```
  port( CLOCK : STD_LOGIC;
```

```
        WR : IN STD_LOGIC;
```

```
        ADDR_BUS : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
```

```
        IN_DATA_BUS : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
```

```
        OUT_DATA_BUS : OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
```

```
end RAM;
```

```
architecture RAM_arch of RAM is
```

```
  type ram_type is array (3 downto 0) of STD_LOGIC_VECTOR(7 downto 0);
```

```
  signal UNIT : ram_type;
```

```
begin
```

```
  process(CLOCK, ADDR_BUS, UNIT)
```

```
  begin
```

```
    if (rising_edge(CLOCK)) then
```

```
      if (WR = '1') then
```

```
        UNIT(conv_integer(ADDR_BUS)) <= IN_DATA_BUS;
```

```
      end if;
```

```
    end if;
```

```
    OUT_DATA_BUS <= UNIT(conv_integer(ADDR_BUS));
```

```
  end process;
```

```
end RAM_arch;
```

Файл SEG_DECODER.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

entity BIN_TO_BCD is

```
port( CLOCK : IN STD_LOGIC;
      RESET : IN STD_LOGIC;
      ACC_DATA_OUT_BUS : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
      COMM_ONES      : OUT STD_LOGIC;
      COMM_DECS      : OUT STD_LOGIC;
      COMM_HUNDREDS  : OUT STD_LOGIC;
      SEG_A  : OUT STD_LOGIC;
      SEG_B  : OUT STD_LOGIC;
      SEG_C  : OUT STD_LOGIC;
      SEG_D  : OUT STD_LOGIC;
      SEG_E  : OUT STD_LOGIC;
      SEG_F  : OUT STD_LOGIC;
      SEG_G  : OUT STD_LOGIC;
      DP    : OUT STD_LOGIC);
end BIN_TO_BCD;
```

architecture Behavioral of BIN_TO_BCD is

```
signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0001";
signal HONDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
```

begin

```
BIN_TO_BCD : process (ACC_DATA_OUT_BUS)
    variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;
    variable bcd     : STD_LOGIC_VECTOR(11 downto 0) ;
begin
    bcd      := (others => '0') ;
    hex_src  := ACC_DATA_OUT_BUS;
```

```
    for i in hex_src'range loop
        if bcd(3 downto 0) > "0100" then
            bcd(3 downto 0) := bcd(3 downto 0) + "0011" ;
        end if ;
        if bcd(7 downto 4) > "0100" then
            bcd(7 downto 4) := bcd(7 downto 4) + "0011" ;
        end if ;
        if bcd(11 downto 8) > "0100" then
            bcd(11 downto 8) := bcd(11 downto 8) + "0011" ;
        end if ;
```

```

        bcd := bcd(10 downto 0) & hex_src(hex_src'left) ; -- shift bcd + 1 new
entry
        hex_src := hex_src(hex_src'left - 1 downto hex_src'right) & '0' ; --
shift src + pad with 0
    end loop ;

    HONDREDS_BUS    <= bcd (11 downto 8);
    DECS_BUS        <= bcd (7 downto 4);
    ONES_BUS         <= bcd (3 downto 0);

end process BIN_TO_BCD;

INDICATE : process(CLOCK)
type DIGIT_TYPE is (ONES, DECS, HUNDREDS);

variable CUR_DIGIT    : DIGIT_TYPE := ONES;
variable DIGIT_VAL     : STD_LOGIC_VECTOR(3 downto 0) := "0000";
variable DIGIT_CTRL    : STD_LOGIC_VECTOR(6 downto 0) :=
"0000000";
variable COMMONS_CTRL : STD_LOGIC_VECTOR(2 downto 0) :=
"000";

begin
    if (rising_edge(CLOCK)) then
        if(RESET = '0') then
            case CUR_DIGIT is
                when ONES =>
                    DIGIT_VAL := ONES_BUS;
                    CUR_DIGIT := DECS;
                    COMMONS_CTRL := "001";
                when DECS =>
                    DIGIT_VAL := DECS_BUS;
                    CUR_DIGIT := HUNDREDS;
                    COMMONS_CTRL := "010";
                when HUNDREDS =>
                    DIGIT_VAL := HONDREDS_BUS;
                    CUR_DIGIT := ONES;
                    COMMONS_CTRL := "100";
                when others =>
                    DIGIT_VAL := ONES_BUS;
                    CUR_DIGIT := ONES;
                    COMMONS_CTRL := "000";
            end case;
        end if;
    end if;
end process;

```

```

end case;

case DIGIT_VAL is          --abcdefg
  when "0000" => DIGIT_CTRL := "1111110";
  when "0001" => DIGIT_CTRL := "0110000";
  when "0010" => DIGIT_CTRL := "1101101";
  when "0011" => DIGIT_CTRL := "1111001";
  when "0100" => DIGIT_CTRL := "0110011";
  when "0101" => DIGIT_CTRL := "1011011";
  when "0110" => DIGIT_CTRL := "1011111";
  when "0111" => DIGIT_CTRL := "1110000";
  when "1000" => DIGIT_CTRL := "1111111";
  when "1001" => DIGIT_CTRL := "1111011";
  when others => DIGIT_CTRL := "0000000";
end case;
else
  DIGIT_VAL := ONES_BUS;
  CUR_DIGIT := ONES;
  COMMONS_CTRL := "000";
end if;

COMM_ONES    <= COMMONS_CTRL(0);
COMM_DECS    <= COMMONS_CTRL(1);
COMM_HUNDREDS <= COMMONS_CTRL(2);

SEG_A <= DIGIT_CTRL(6);
SEG_B <= DIGIT_CTRL(5);
SEG_C <= DIGIT_CTRL(4);
SEG_D <= DIGIT_CTRL(3);
SEG_E <= DIGIT_CTRL(2);
SEG_F <= DIGIT_CTRL(1);
SEG_G <= DIGIT_CTRL(0);
DP  <= '0';

end if;
end process INDICATE;

end Behavioral;

```

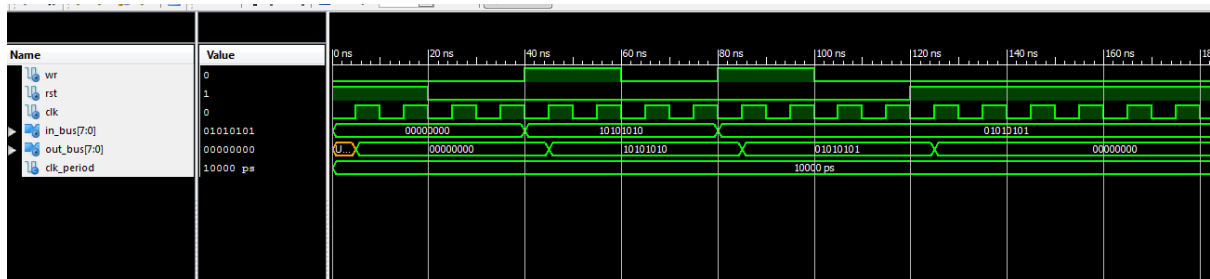


Рис. 2 – Часова діаграма ACC

 


Рис. 3 – Часова діаграма ALU

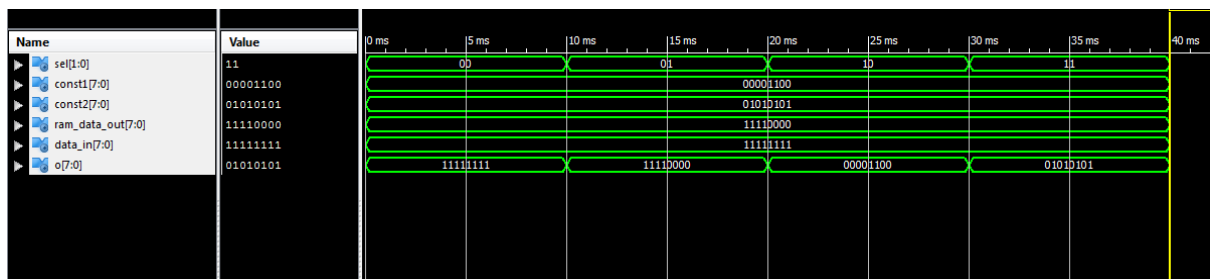


Рис. 4 – Часова діаграма MUX

 


Рис. 5 – Часова діаграма RAM

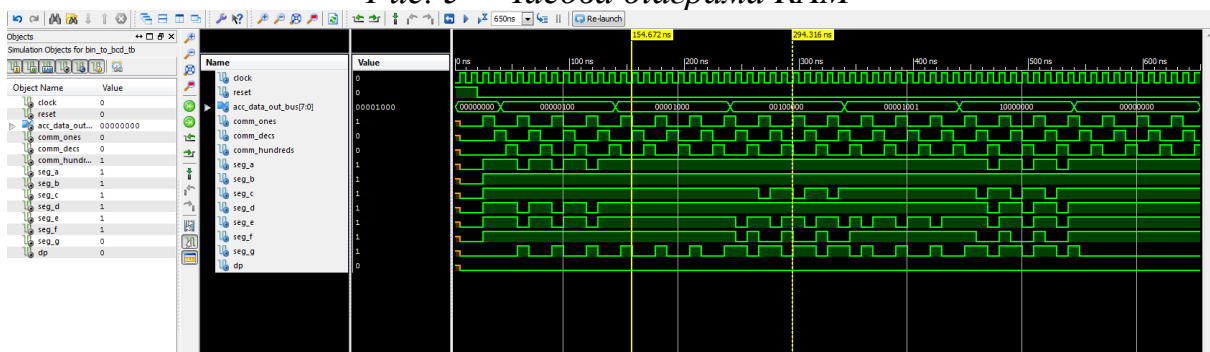


Рис 6. – Часова діаграма SEG_DECODER

 


Рис. 7. – Часова діаграма TopLevel

Файл TopLevelTest.vhd

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.numeric_std.ALL;

LIBRARY UNISIM;

USE UNISIM.Vcomponents.ALL;

ENTITY TOP_SCHEME_TOP_SCHEME_sch_tb IS

END TOP_SCHEME_TOP_SCHEME_sch_tb;

ARCHITECTURE behavioral OF TOP_SCHEME_TOP_SCHEME_sch_tb IS

COMPONENT TOP_SCHEME

PORT(CLOCK : IN STD_LOGIC;

RESET : IN STD_LOGIC;

ENTER_OP1 : IN STD_LOGIC;

ENTER_OP2 : IN STD_LOGIC;

CALCULATE : IN STD_LOGIC;

ACC_OUT_BUS : OUT STD_LOGIC_VECTOR (7 DOWNT0 0);

COM_0 : OUT STD_LOGIC;

COM_1 : OUT STD_LOGIC;

COM_2 : OUT STD_LOGIC;

SEG_A : OUT STD_LOGIC;

SEG_B : OUT STD_LOGIC;

SEG_C : OUT STD_LOGIC;

SEG_D : OUT STD_LOGIC;

SEG_E : OUT STD_LOGIC;

SEG_F : OUT STD_LOGIC;

SEG_G : OUT STD_LOGIC;

DP : OUT STD_LOGIC;

DATA_IN : IN STD_LOGIC_VECTOR (7 DOWNT0 0);

OVERFLOW : OUT STD_LOGIC);

END COMPONENT;

```

SIGNAL CLOCK : STD_LOGIC;
SIGNAL RESET : STD_LOGIC;
SIGNAL ENTER_OP1 : STD_LOGIC;
SIGNAL ENTER_OP2 : STD_LOGIC;
SIGNAL CALCULATE : STD_LOGIC;
SIGNAL COM_0 : STD_LOGIC;
SIGNAL COM_1 : STD_LOGIC;
SIGNAL COM_2 : STD_LOGIC;
SIGNAL SEG_A : STD_LOGIC;
SIGNAL SEG_B : STD_LOGIC;
SIGNAL SEG_C : STD_LOGIC;
SIGNAL SEG_D : STD_LOGIC;
SIGNAL SEG_E : STD_LOGIC;
SIGNAL SEG_F : STD_LOGIC;
SIGNAL SEG_G : STD_LOGIC;
SIGNAL DP : STD_LOGIC;
SIGNAL DATA_IN : STD_LOGIC_VECTOR (7 DOWNTO 0);
SIGNAL ACC_OUT_BUS : STD_LOGIC_VECTOR (7 DOWNTO 0);
SIGNAL TEST : STD_LOGIC_VECTOR (15 DOWNTO 0);
SIGNAL OVERFLOW : STD_LOGIC;

```

constant CLKP: time := 11 ms;

BEGIN

```

UUT: TOP_SCHEME PORT MAP(
  CLOCK => CLOCK,
  RESET => RESET,
  ENTER_OP1 => ENTER_OP1,
  ENTER_OP2 => ENTER_OP2,
  CALCULATE => CALCULATE,
  COM_0 => COM_0,
  COM_1 => COM_1,
  COM_2 => COM_2,
  SEG_A => SEG_A,
  SEG_B => SEG_B,
  SEG_C => SEG_C,
  SEG_D => SEG_D,
  SEG_E => SEG_E,
  SEG_F => SEG_F,
  SEG_G => SEG_G,
  DP => DP,
  DATA_IN => DATA_IN,

```



```

    ACC_OUT_BUS => ACC_OUT_BUS,
    OVERFLOW => OVERFLOW
);

CLOCK_process: process
begin
    CLOCK <= '0';
    wait for 41500 ps;
    CLOCK <= '1';
    wait for 41500 ps;
end process;

-- * Test Bench - User Defined Section *
tb : PROCESS
BEGIN

    lp1: for i in 2 to 2 loop
        lp2: for j in 5 to 5 loop
            TEST <=
std_logic_vector(to_unsigned((((to_integer(unsigned(std_logic_vector(to_unsi
gned(i, 8))))* 2 * to_integer(unsigned(std_logic_vector(to_unsigned(j, 8))))
+ to_integer(unsigned(std_logic_vector(to_unsigned(i, 8)))) + 10), 16));
            ENTER_OP1 <= '1';
            ENTER_OP2 <= '1';
            CALCULATE <= '1';
            DATA_IN <= (others => '0');
            RESET <= '0';
            wait for CLKP;
            RESET <= '1';
            wait for CLKP;
            DATA_IN <= (std_logic_vector(to_unsigned(i, 8))); -- A
            ENTER_OP1 <= '0';
            wait for CLKP;
            ENTER_OP1 <= '1';
            wait for CLKP * 2;
            DATA_IN <= (std_logic_vector(to_unsigned(j, 8))); -- B
            ENTER_OP2 <= '0';
            wait for CLKP;
            ENTER_OP2 <= '1';
            wait for CLKP * 2;
            CALCULATE <= '0'; -- START CALCULATION
            REPORT "OP1 = (" & integer'image(i) & ") and OP2 = (" &
integer'image(j) & ") calculation started" SEVERITY NOTE;

```

```
wait for CLKP * 7;  
assert ACC_OUT_BUS = TEST(7 DOWNT0 0) severity FAILURE;  
REPORT "OP1 = (" & integer'image(i) & ") and OP2 = (" &  
integer'image(j) & ") calculation finished" SEVERITY NOTE;  
wait for CLKP;  
end loop;  
end loop;  
WAIT; -- will wait forever  
END PROCESS;  
-- *** End Test Bench - User Defined Section ***  
  
END;
```

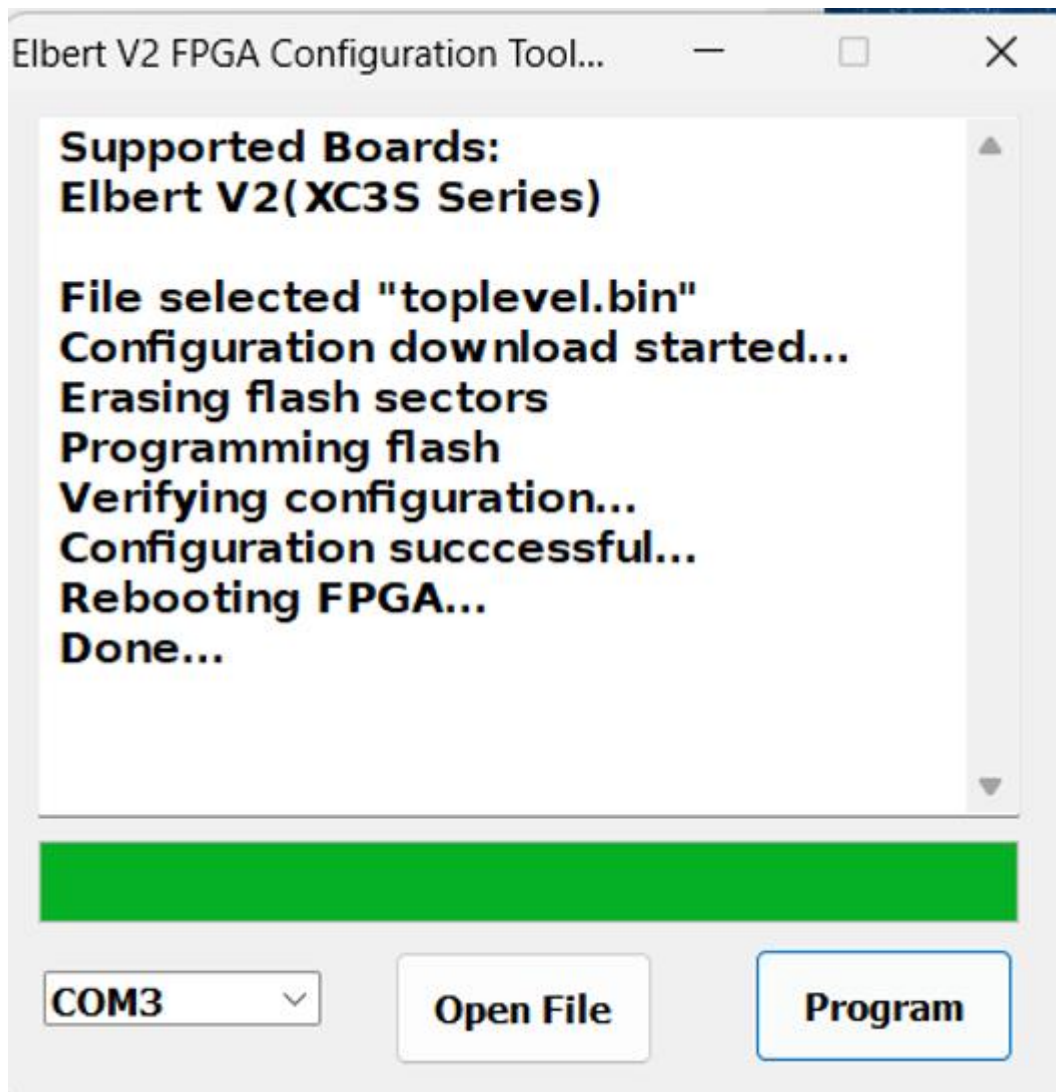


Рис.9 – Успішна прошивка

Висновок: Виконуючи дану лабораторну роботу я навчився реалізовувати цифровий автомат для обчислення значення виразів використовуючи засоби VHDL.